

MD TANVEER ALAM

20JEOSS7

Experiment - 5

Title:- Study the parallel operation of two three-phase transformers belonging to same vector groups.

Objective:- To check the vector groups of two three-phase transformers and to operate them in parallel.

Apparatus Required:-

S.No.	Name	Quantity	Range	Maker's Name
1.	3- ϕ Transformer.	2	3KVA	Concept. Int.
2.	3- ϕ Auto Transformer.	1	32A(0-220V)	Cosapt. Int.
3.	Digital phase angle meter.	1	(0-360°)	Concept Int.
4.	M.C.B.	1	-	-

Theory:- The need for parallel operation of three-phase transformers arises more frequently, since the generation, transmission, & distribution of power is always three phase. The advantages of using two or more transformers in parallel over the use of one large unit, are (i) the power system becomes more reliable. (ii) Transformers can be switched off or on, depending upon the power demand. (iii) The cost of stand by unit is much less when two or more transformers are installed. The various conditions which must be fulfilled for the satisfactory parallel operation of two or more transformers, are as follows, (i) same voltage ratio, (ii) same polarity, (iii) same phase sequence and (iv) same phase shift.

Three-phase transformers may have the following four standard connections.

- | | |
|-------------------------------------|-------------------------------|
| (a) Star-Delta ($Y-\Delta$) | (b) Delta-Star ($\Delta-Y$) |
| (c) Delta-Delta ($\Delta-\Delta$) | (d) Star-Star ($Y-Y$) |

A bank of three transformers or a three-phase transformer may have its primary & secondary windings connected in star, delta or zig-zag. The choice of particular connections depends upon the service conditions. In representing a three-phase transformer, the high voltage (H.V) winding is indicated by a capital letter (e.g. Y for star, Δ for Delta) and low voltage (L.V) winding by a lower case letter (e.g. y for star & d for Delta). The symbol " Yd " represents a three-phase transformer with hv in star & lv in delta. In the various transformer connections, the hv line end & corresponding lv line end may or may not have a phase displacement between them. This time phase displacement can be expressed either in degrees or by a much more convenient method known as a clock method of circle designation. According to this method, the hv line phase is considered as the minute hand always set at 12 O'clock (zero hour) position & the corresponding lv line phase represented by hour hand. For two winding three-phase transformers, as per the clock method, first symbol represents hv & lv line ends expressed as clock hour number. For example, symbol " $Yd11$ " represents a polyphase transformer with hv winding in star, lv winding in delta & the lv line

Circuit Diagram:-

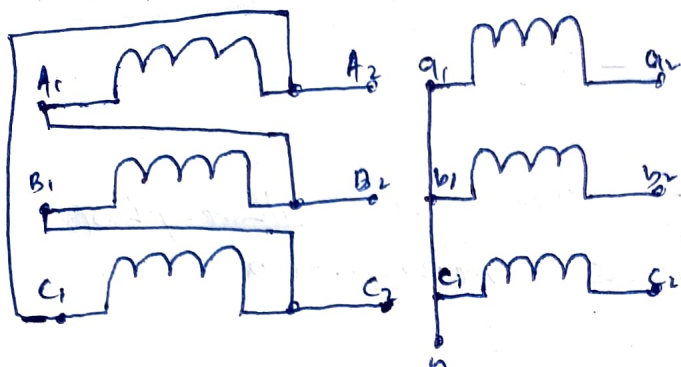


Fig 1. Dy11 arrangement

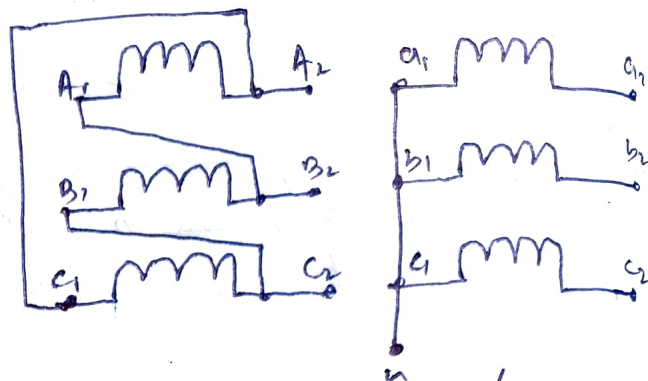


Fig 2. Dy11 arrangement

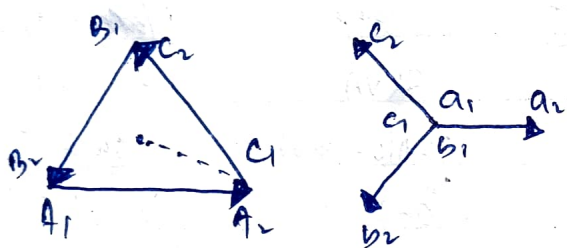


Fig 3. Phasor Diagram of Dy11

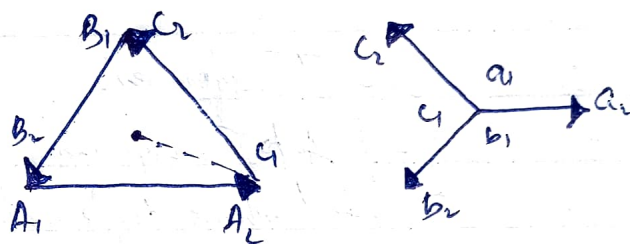


Fig 4. Phasor Diagram of Dy11

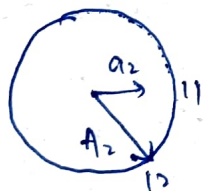


Fig 5. Clock diagram of Dy11

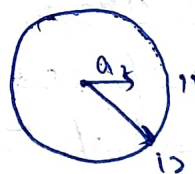


Fig 6. Clock diagram of Dy11

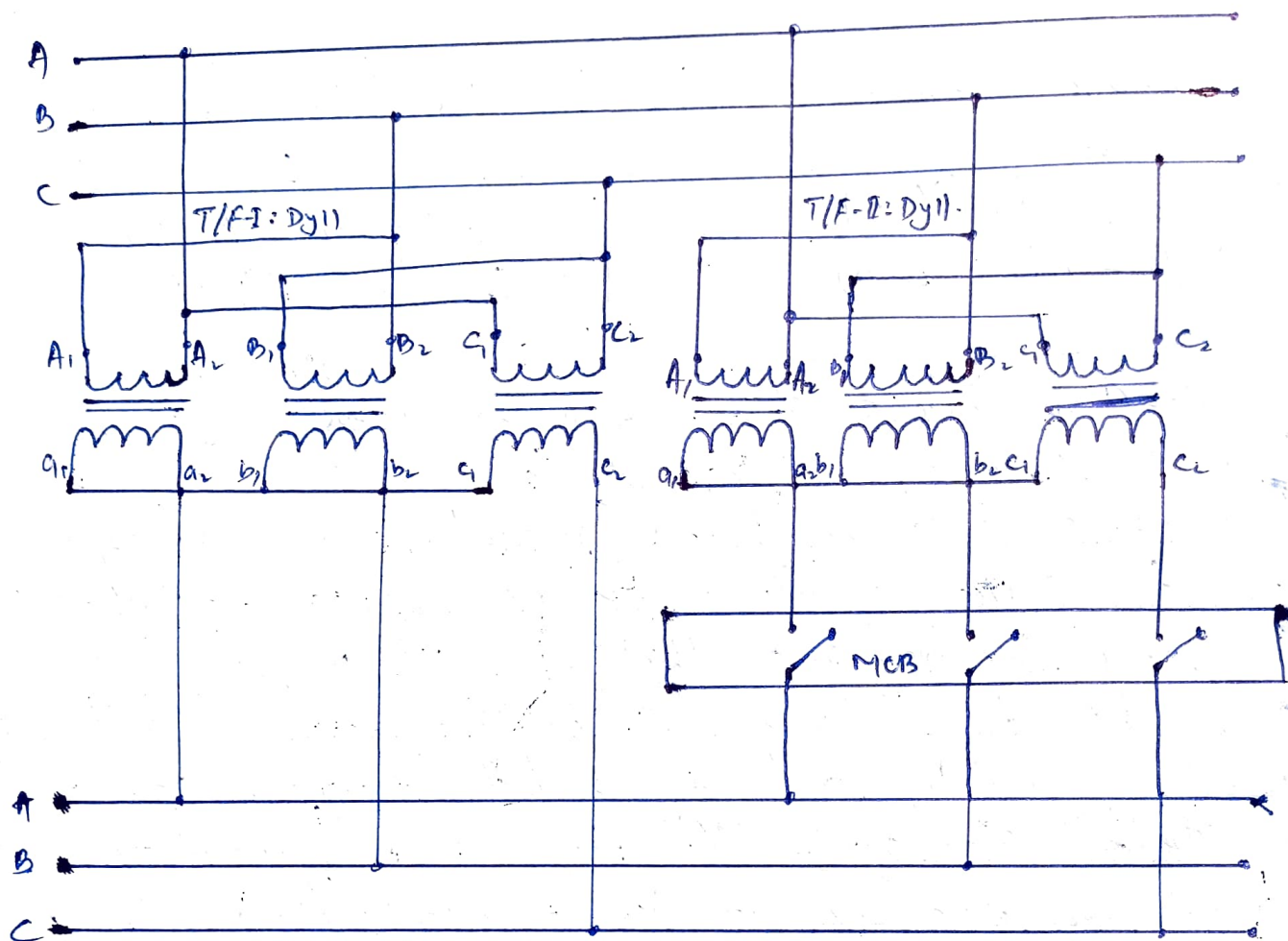


Fig. 7: Connection diagram for parallel operation of two three phase transformers belonging to same vector group.

phases at 11 o'clock, i.e., 30° ahead of the zero line position of the LV line phases.

Vector group: Vector group denotes for how much angle line to neutral voltage of LV side lead or lag LV line to neutral voltage of HV side. Vector groups can be divided into four groups as follows

- (a) Group No. 1 (0° phase displacement): $Yy0^\circ$ or $Yy12$, $Dd0^\circ$ or $Dd12$.
- (b) Group No. 2 (180° phase disp.): $Yy180^\circ$ or $Yy6$, $Dd180^\circ$ or $Dd6$.
- (c) Group No. 3 (minus 30° phase disp.): $Yd-30^\circ$ or $Yd1$, $Dy-30^\circ$ or $Dy1$.
- (d) Group No. 4 (plus 30° phase disp.): $Yd+30^\circ$ or $Yd11$, $Dy+30^\circ$ or $Dy11$.

Observation Table:-

Transformer - I : $Dy11$			Transformer - II : $Dy11$		
Line to line voltage HV side	Line to line voltage LV side	Phase angle diff.	Line to line voltage HV side	Line to line voltage LV side	Phase angle diff.
V_{AB}	V_{ab}	327°	V_{AB}	V_{ab}	327°
V_{BC}	V_{bc}	327°	V_{BC}	V_{bc}	327°
V_{CA}	V_{ca}	327°	V_{CA}	V_{ca}	327°

Results:- The parallel operation of two three phase transformers has been performed & studied successfully by checking their voltage phasors.

Precautions:- 1. Loose connections should not be made. (Tight connections).
2. Live wire should not be touched
3. Power supply should be switched off while making connections.